

# BALUNS 101

Learn Just Enough to be Dangerous!

## Important Principle:

- Don't believe anyone who claims to be an expert on baluns.


# First - Some Terms

- **BALUN** comes from “Balanced to Unbalanced”  
This usually means connecting a balanced load such as a dipole antenna to an unbalanced input such as a 50-ohm coaxial cable. The shield side of the cable is usually grounded.
- **BALUNS** can also change impedance levels. For example, 4:1, or  $200\Omega$  to  $50\Omega$  or  $300\Omega$  to  $75\Omega$ .
- **UNUN** means “Unbalanced to Unbalanced”  
This is a device inserted into a coaxial transmission line usually to reduce “common mode” currents - more on that later.


# The BALUN is a Transmission Line Transformer (TLT)

- Some BALUNS are “narrow-band” because they depend on a section of transmission line that is a particular fraction of a wavelength.
- However, most BALUNS are made from short sections of transmission lines (compared to  $\lambda$ ) surrounded by magnetic media with their ends connected to show transformer-like properties. These have much greater bandwidths.
- In many cases the transmissions lines are bifilar or multifilar windings but can be coaxial cable or strip-line cable.

# Differential vs. Common Mode Current

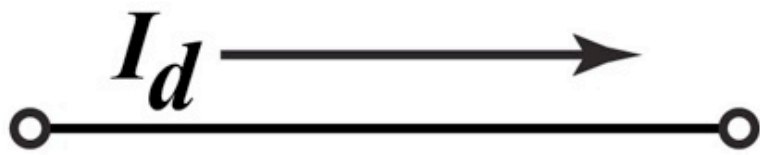


***“Differential” Mode***

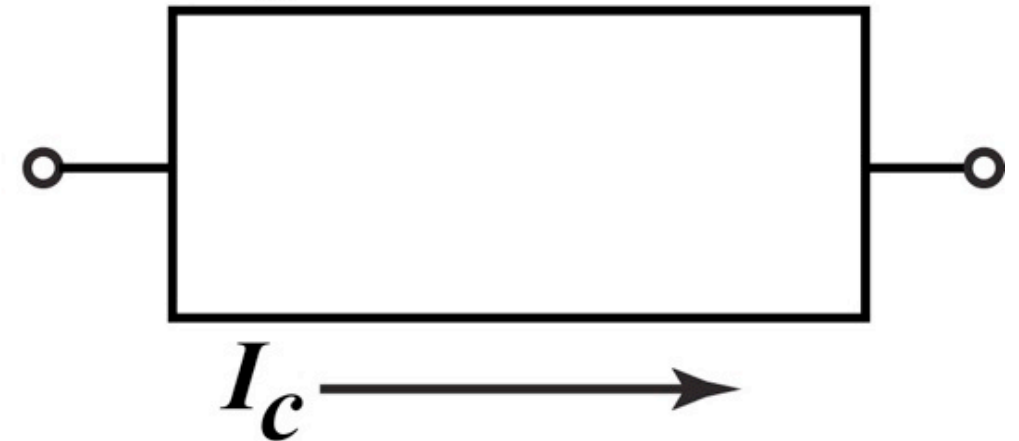


***“Common” Mode***

# Two Types of BALUNS

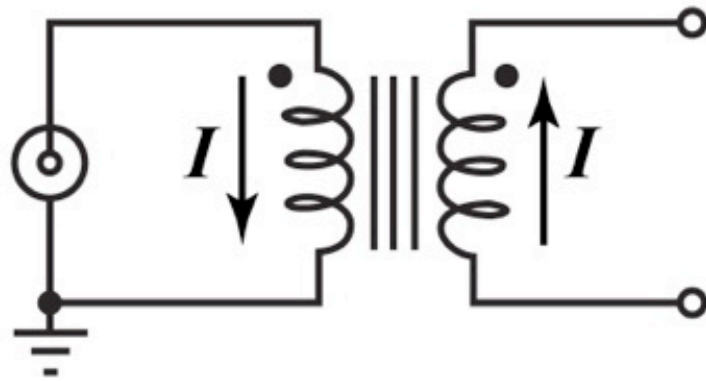


1:1 Voltage Balun

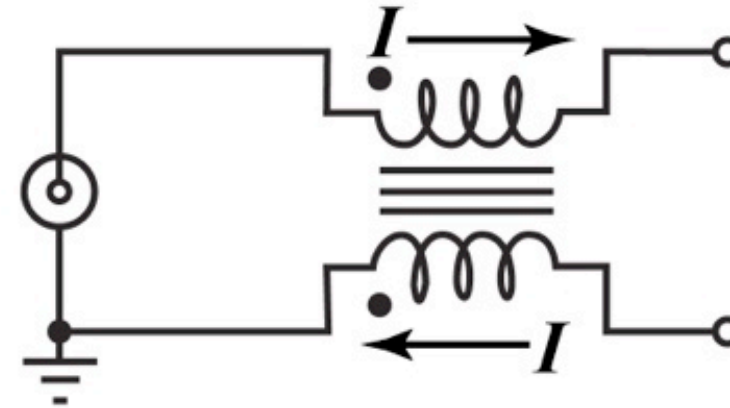

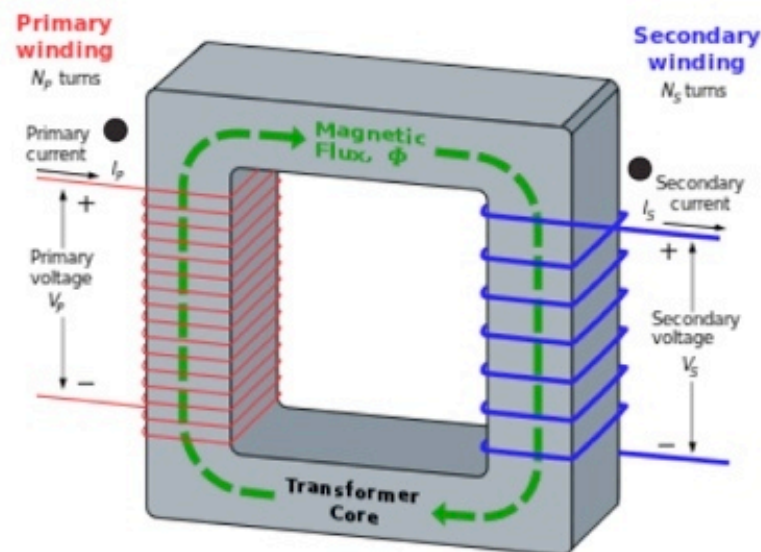
1:1 Current Balun

**Dot Convention:** Positively increasing instantaneous current entering the primary winding's dot end induces positive polarity voltage at the secondary winding's dot end.




**Note:** When building transformers, dotted ends of the windings enter the core center from the same side.

# Two Types of BALUNS

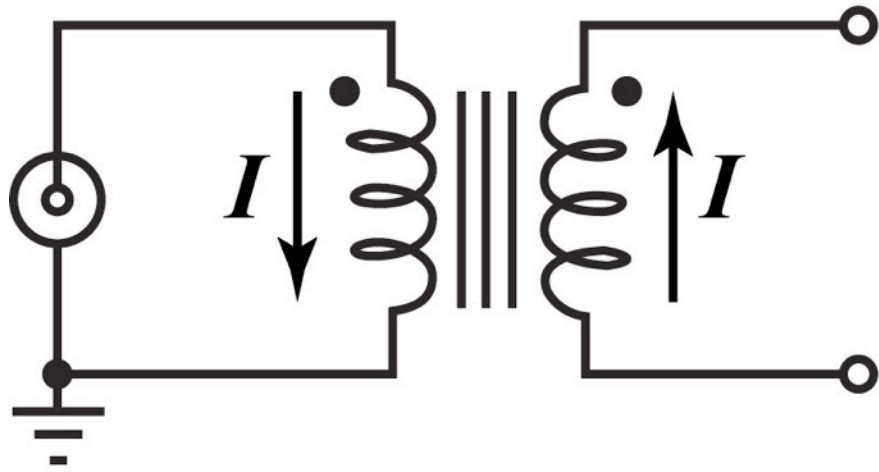


1:1 Voltage Balun

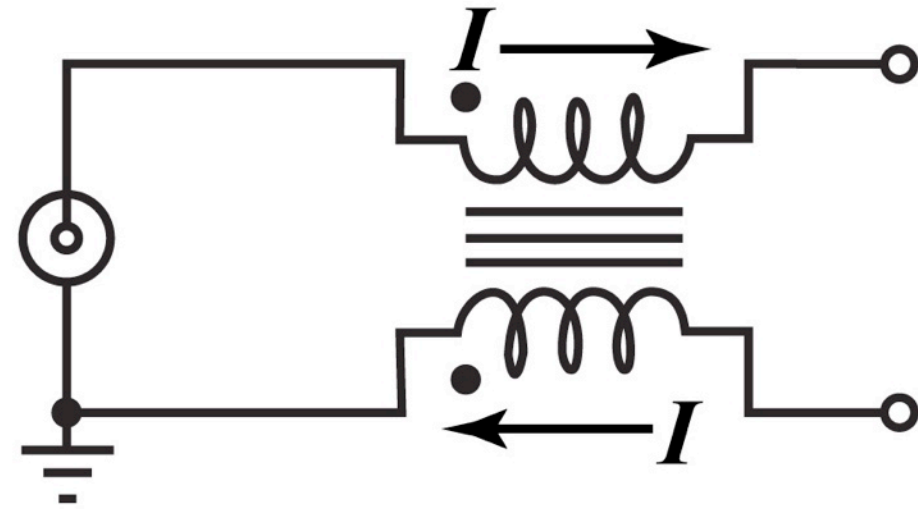

1:1 Current Balun


- Some authors claim that if the impedance ratio is greater than 1:1 it must be a Voltage BALUN.
- However, this does not seem to be true, and Current BALUNs can have different impedance ratios.

# Common Mode Current in a Feed Line

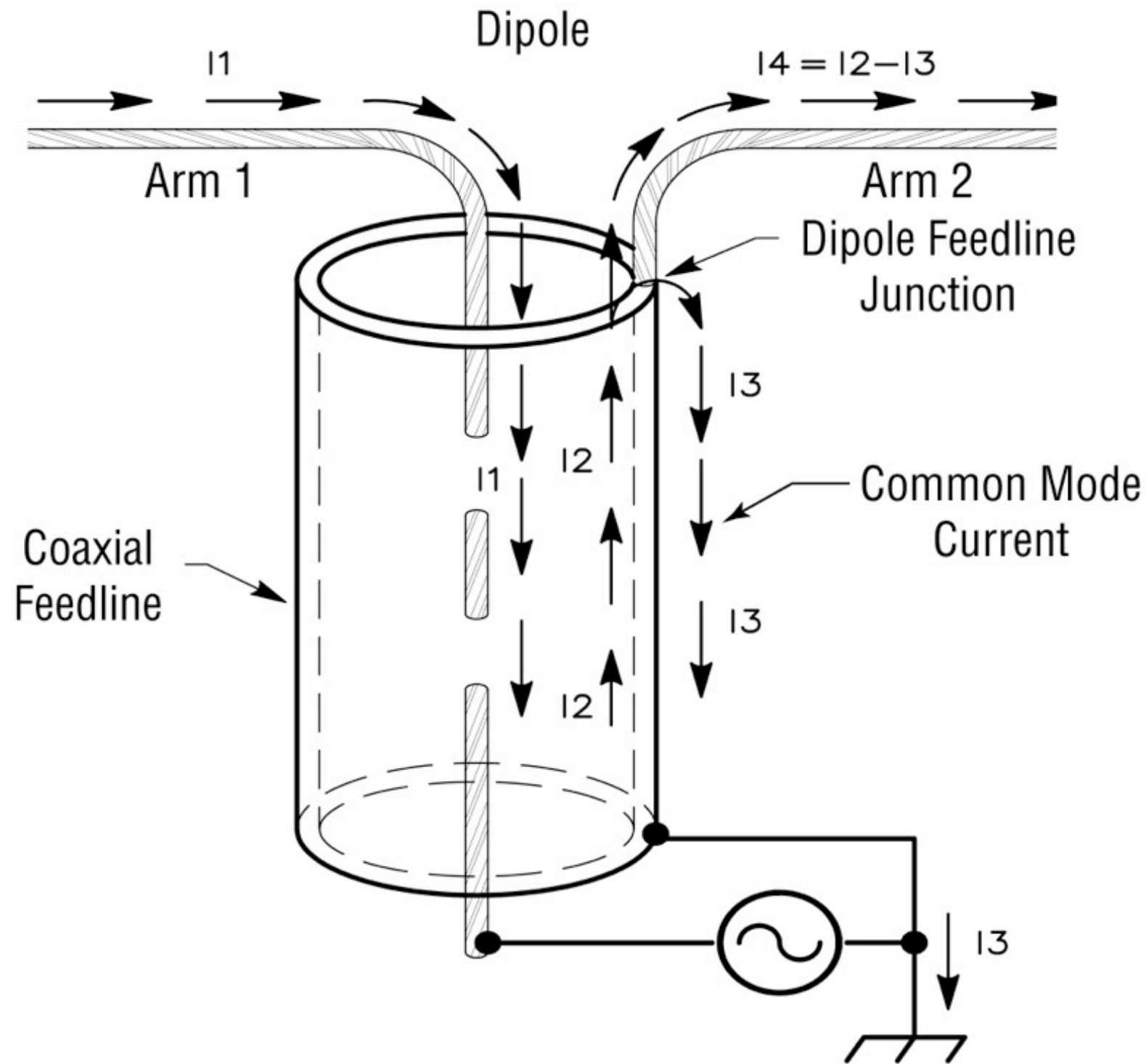

Common Mode Current in Coax can Radiate and Create RFI in Shack
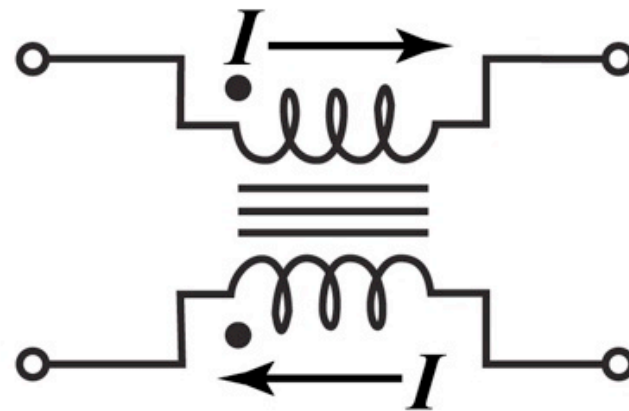
# Current BALUN Opposes Common Mode Currents



1:1 Current Balun


The Current BALUN opposes Common Mode currents.  
Sometimes called a “Choke BALUN.”


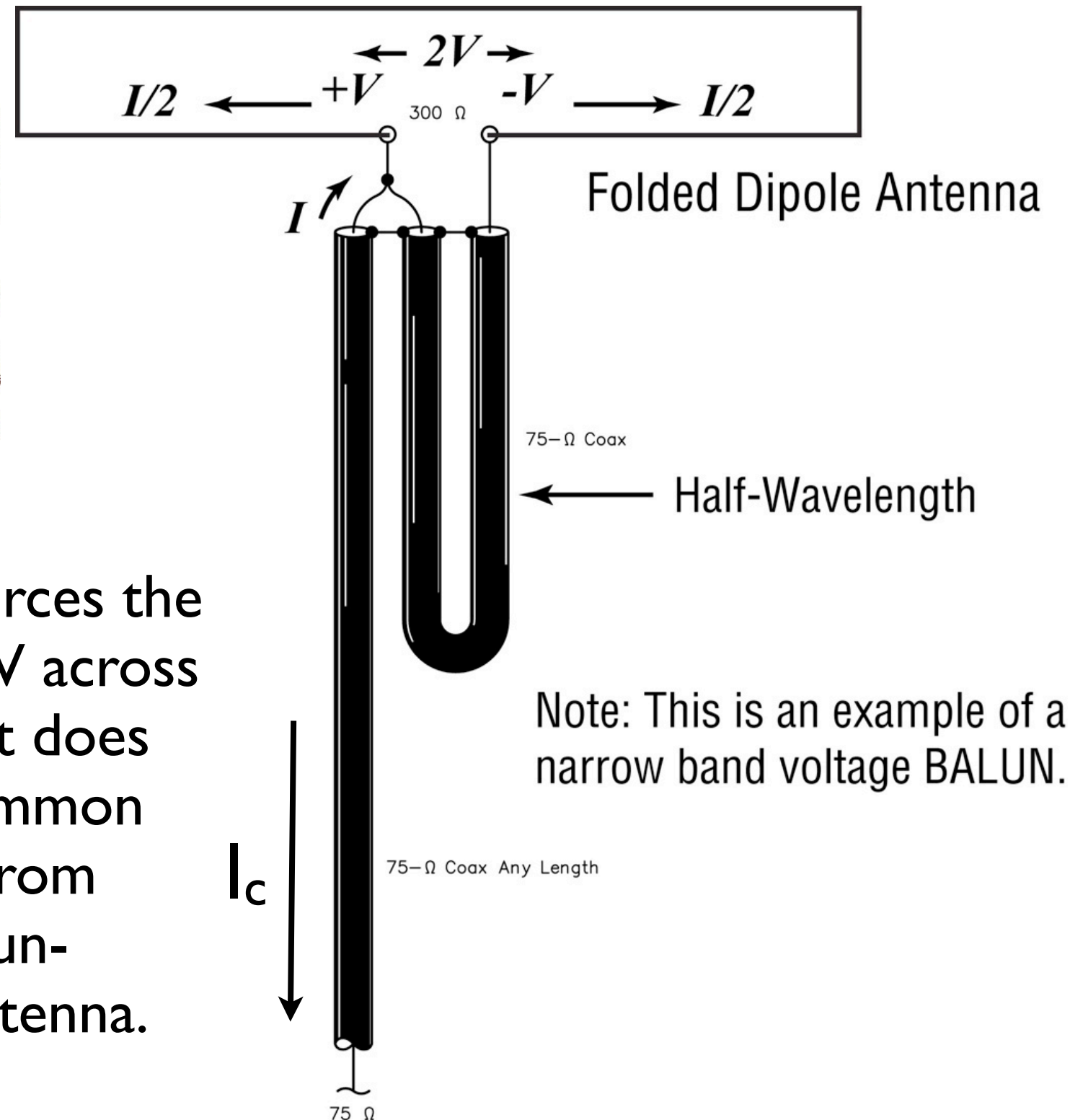
# 4:1 Impedance Transform with Voltage BALUN




This BALUN forces the voltage to be  $2V$  across the antenna, but does not prevent common mode current from factors which “un-balance” the antenna.




Note: This is an example of a narrow band voltage BALUN.

# A Broadband 4:1 Voltage BALUN

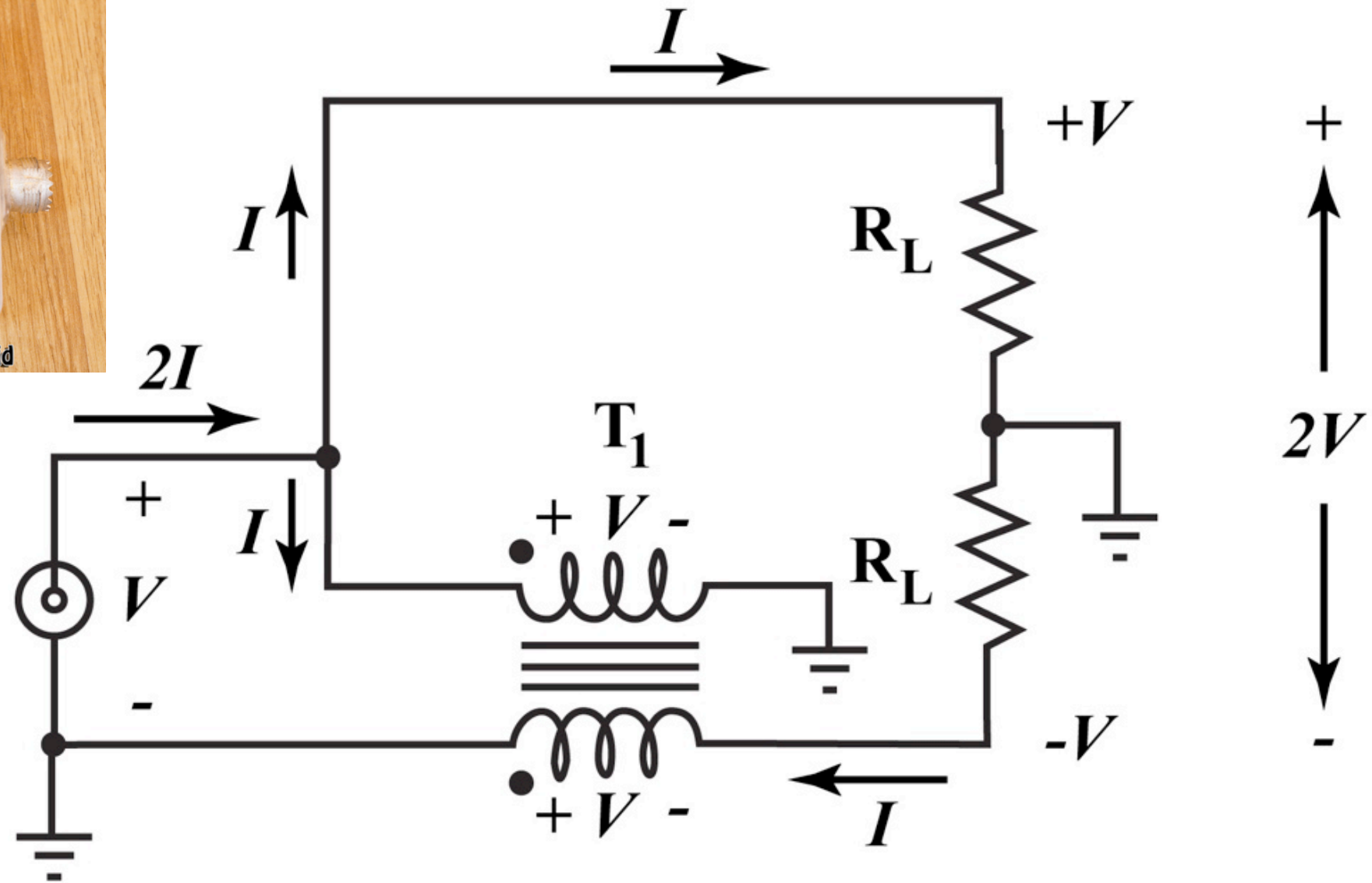

The Ruthroff 4:1 Voltage Balun with Symmetrical Load

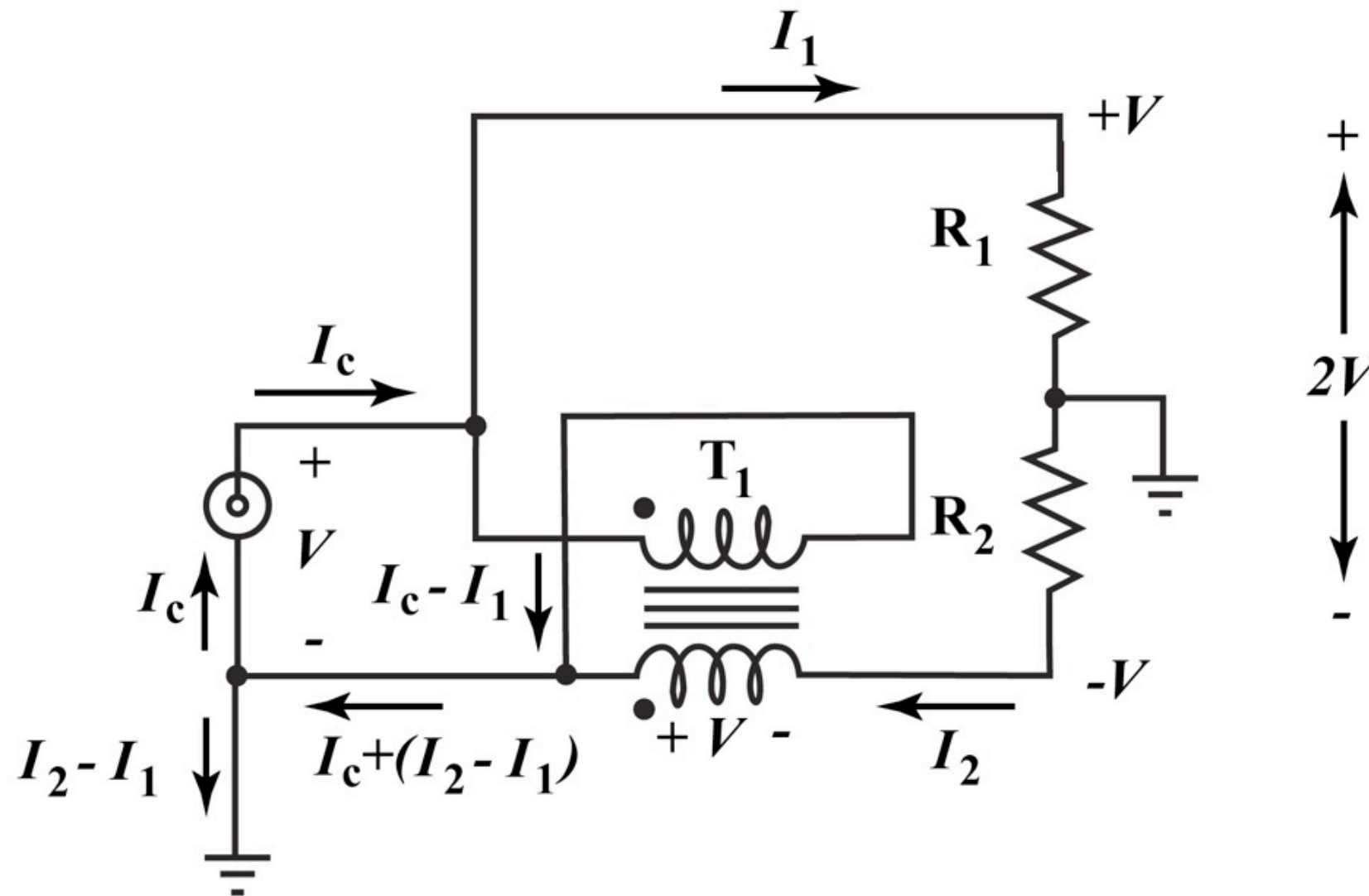
# Ruthroff 4:1 Voltage BALUN with Unbalanced Load



Note: Unless the loads are symmetrical (balanced) and  $I_2 - I_1 = 0$ , some excess current flows through the ground connection as “common mode” current.

# The Ruthroff 4:1 Voltage Balun

# New Carolina Windom Antenna

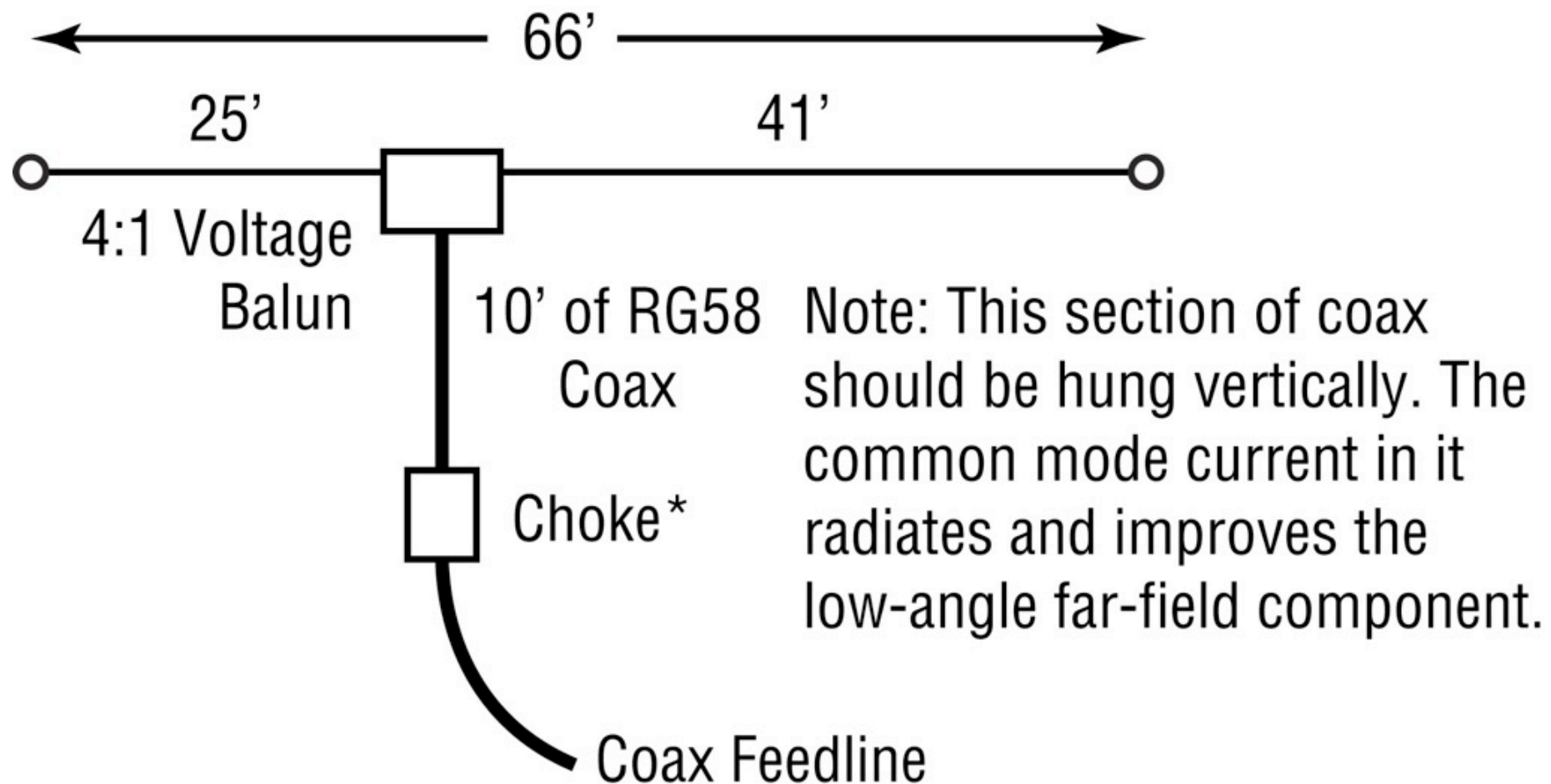


The “New Carolina Windom” Antenna for  
40, 20, 15, and 10 meters

\*The Choke can be made with tubular ferrite cores  
slipped over a short section of coaxial cable.



# Choke UNUNs

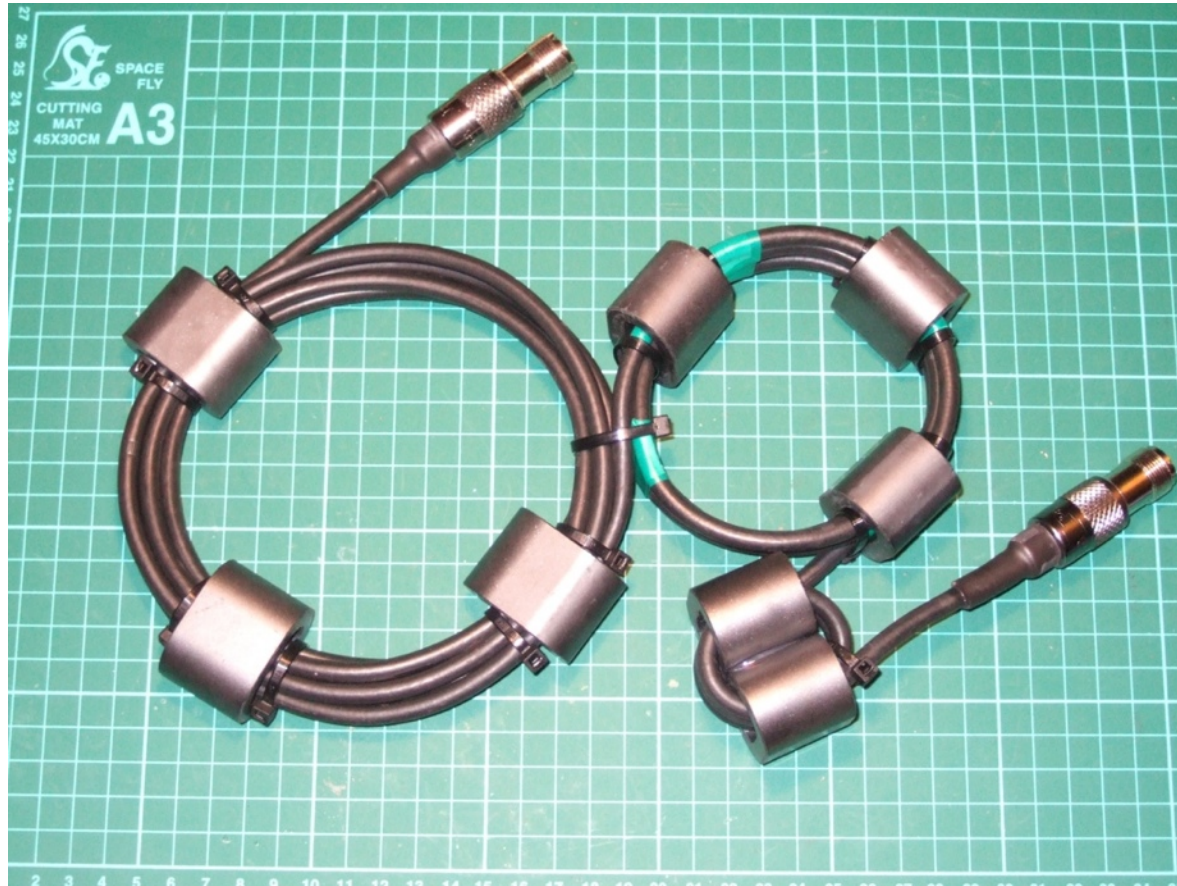




# Choke UNUNs




DX Engineering FCC050-H05-A  
160 to 6 meters, 2kW CW/5kW SSB

# “Ugly” Choke UNUNs

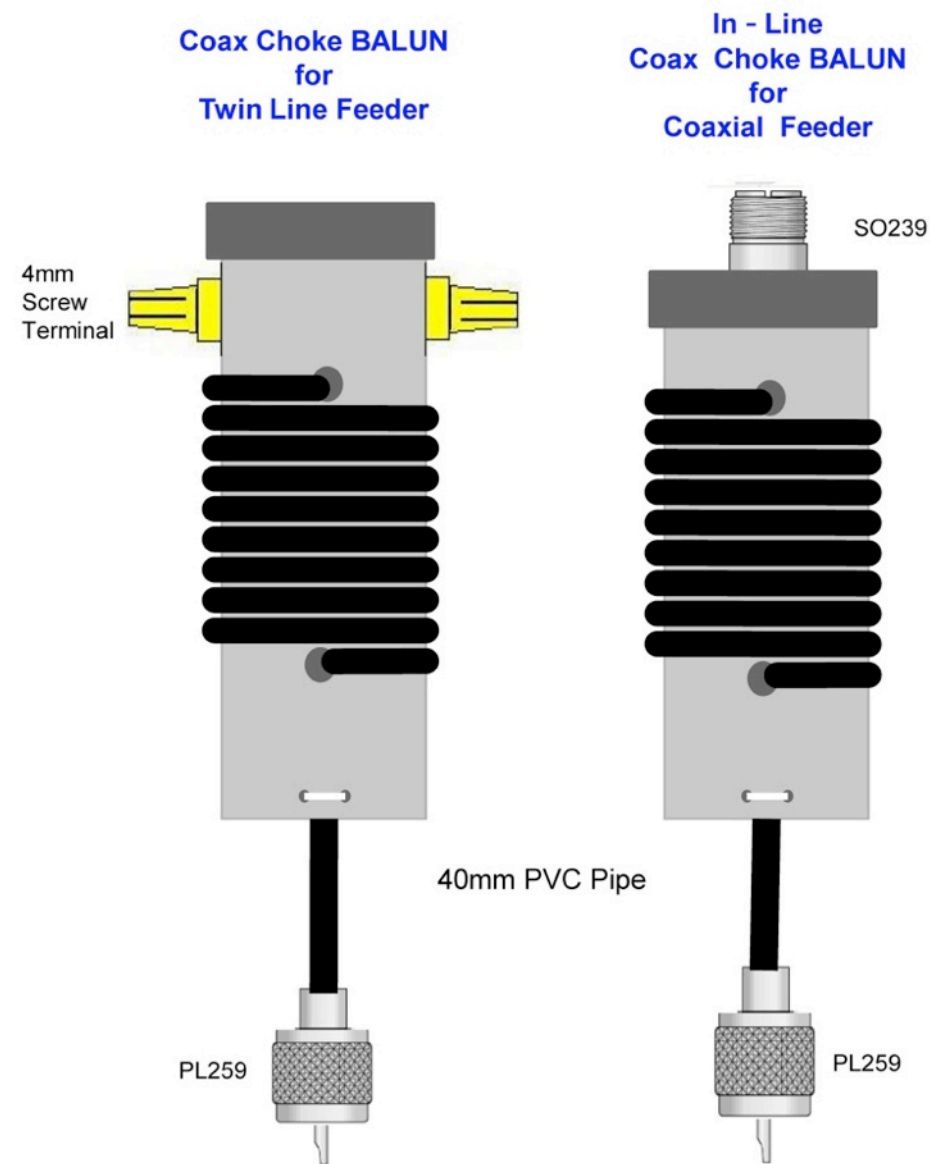


Usually 15 to 22 feet of RG-8 coax wound on a form 4 to 6 inches in diameter.

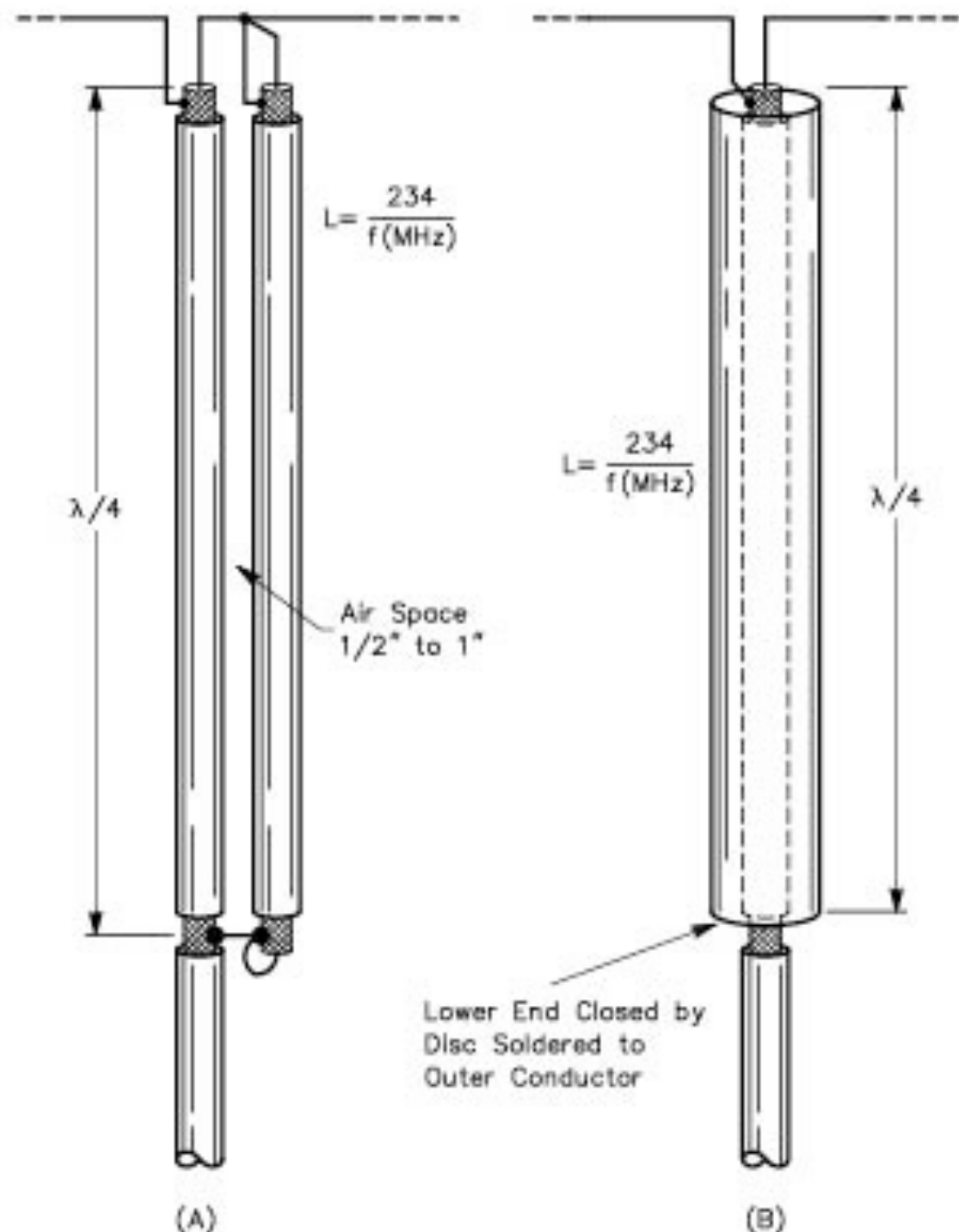

**Fig 35—Fixed-balun methods for balancing the termination when a coaxial cable is connected to a balanced antenna. These baluns work at a single frequency. The balun at B is known as a “sleeve balun” and is often found at VHF.**



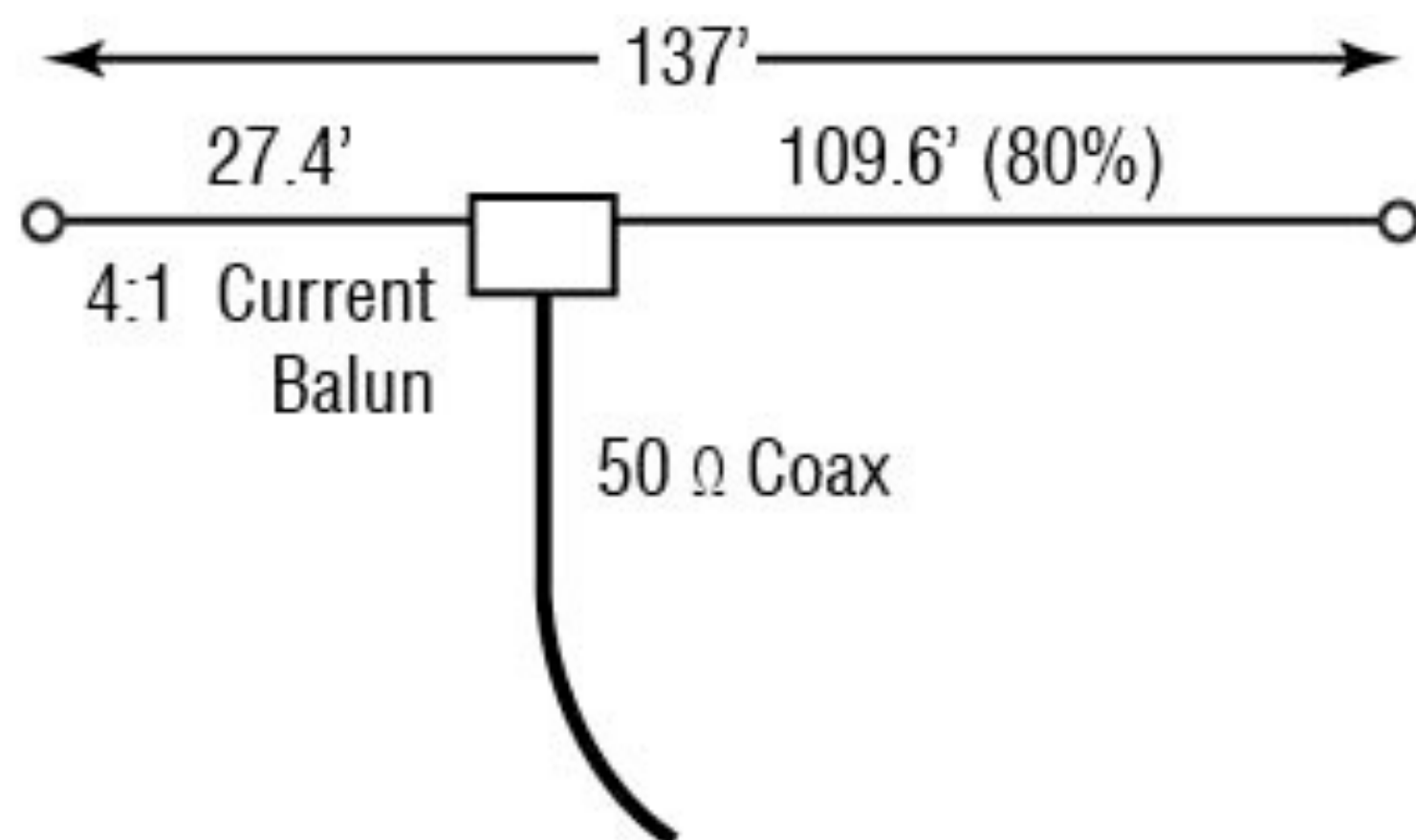


## Off Center Fed (OCF) Dipole (80:20)

Note: I have seen ratios reported of 84:16, 80:20, 66:34, and the “traditional” 62:38.

W8JI claims this antenna has better than 2:1 SWR  
on 80, 40, 30, 20, 15, 12, and 10 meters.


([http://www.w8ji.com/windom\\_off\\_center\\_fed.htm](http://www.w8ji.com/windom_off_center_fed.htm))

# 4:1 Guanella Current BALUN

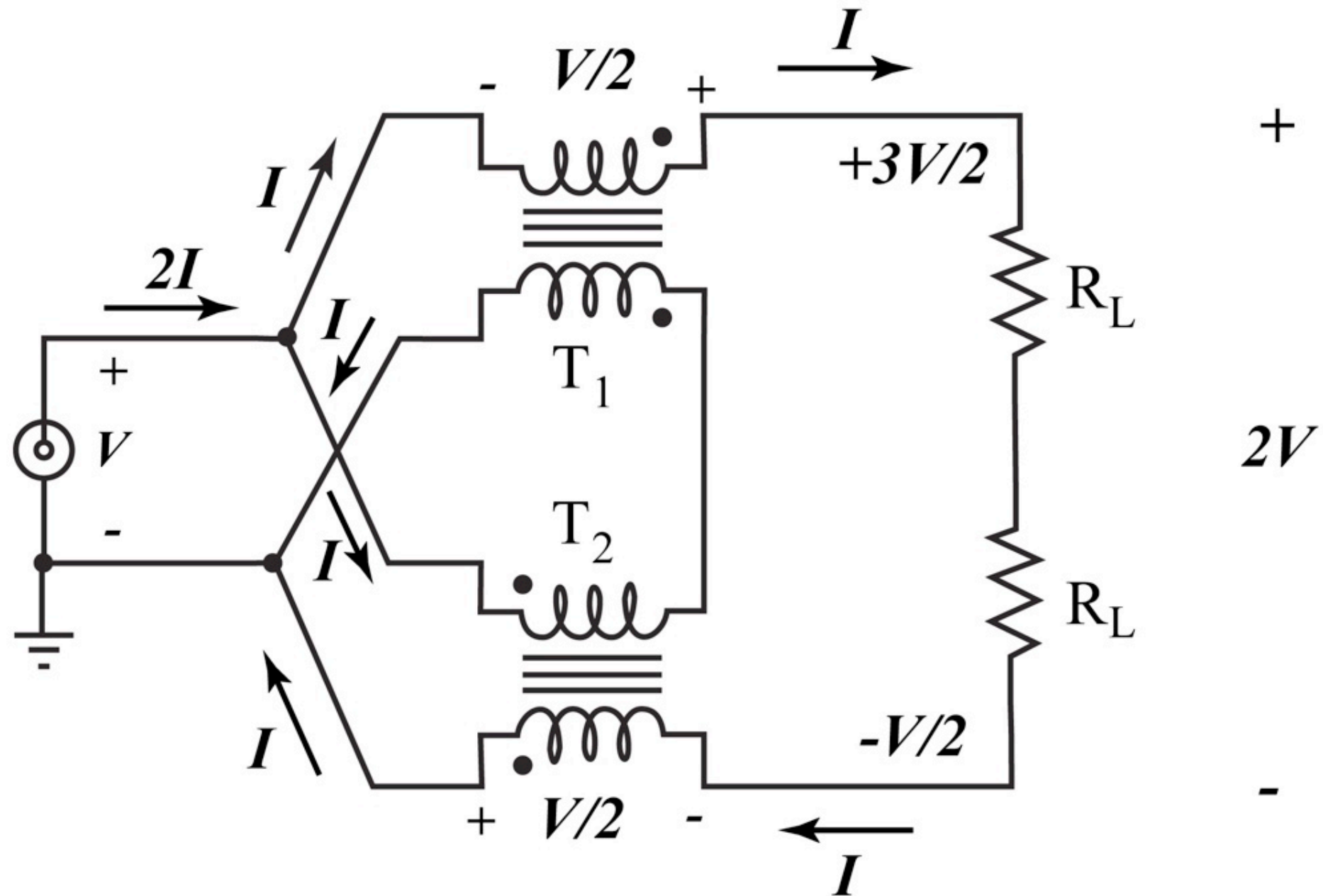


The Guanella 4:1 Current Balun with Floating Load

# 4:1 Guanella Current BALUN

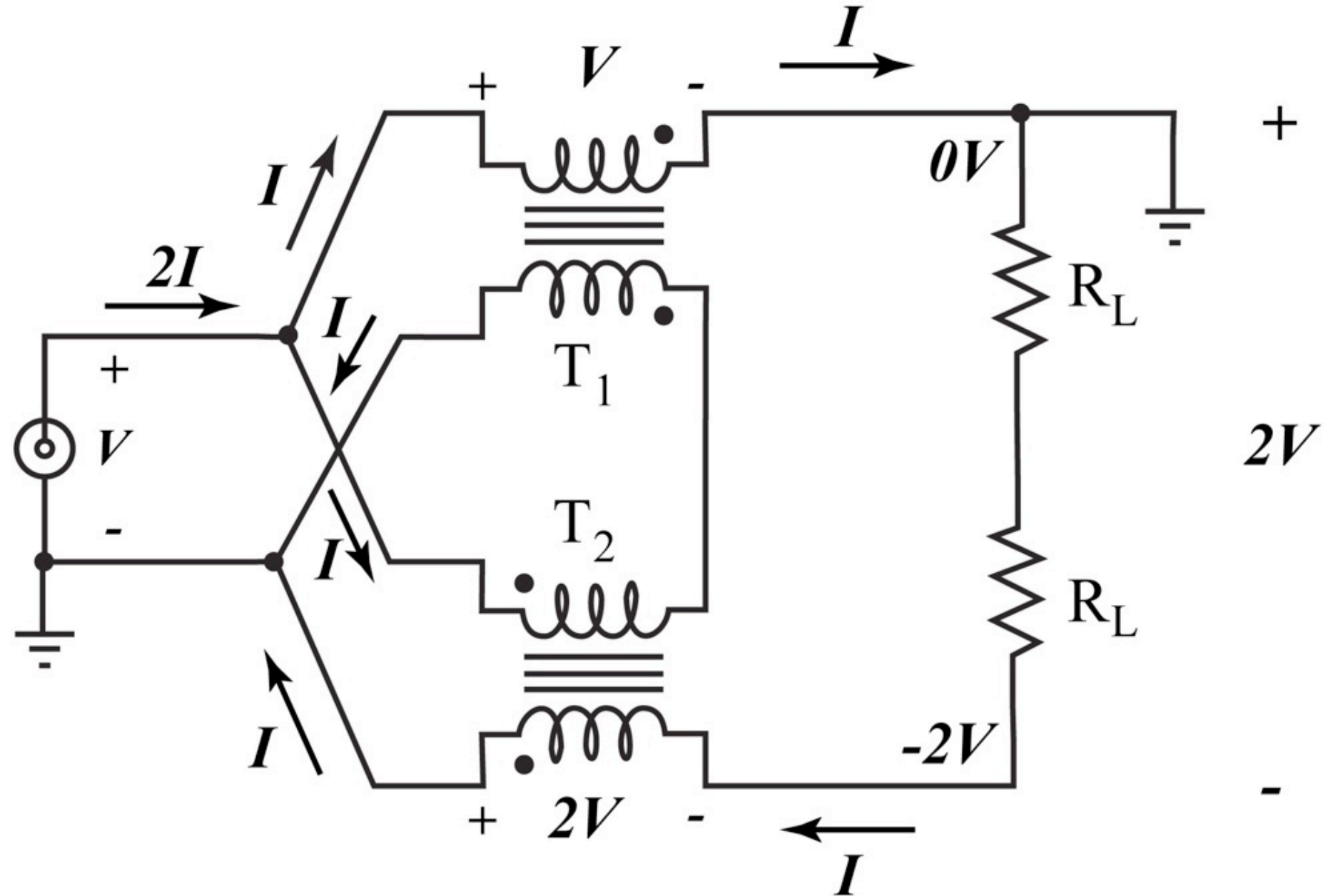


The Guanella 4:1 Current Balun with Unbalanced Load

# 4:1 Guanella Current BALUN

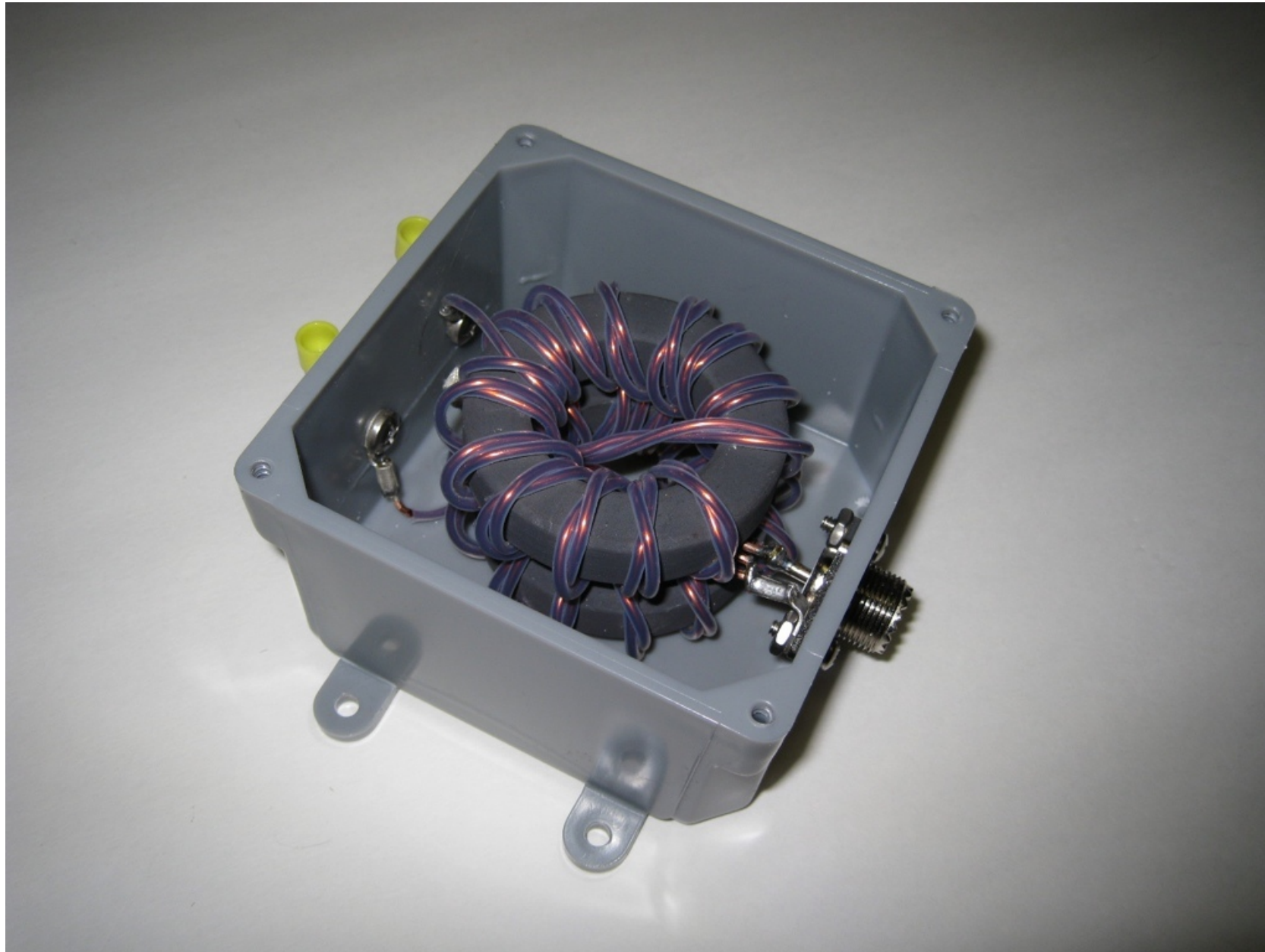

Guanella BALUN should be made with two cores.


# Improved 4:1 Current BALUN

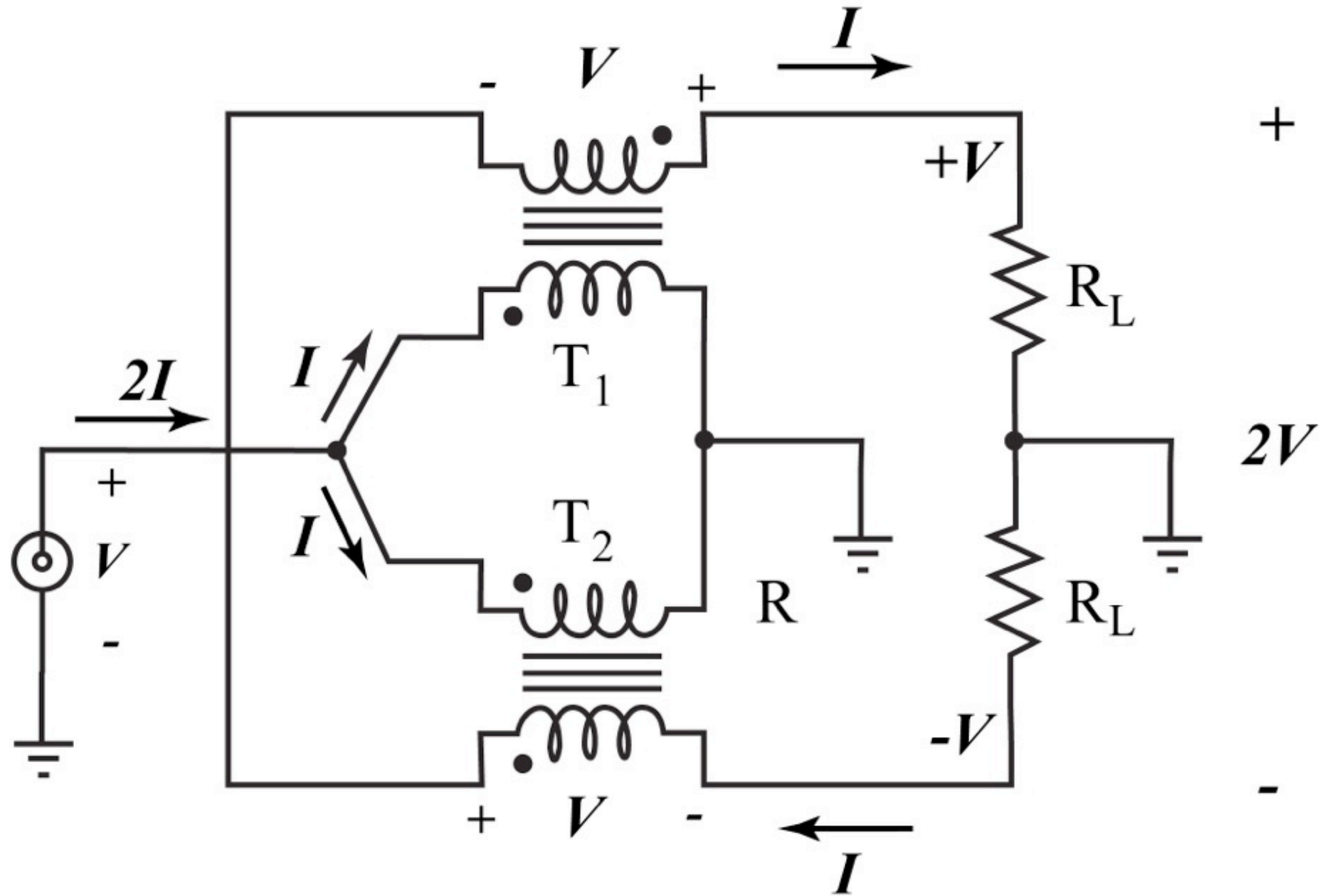

An Improved 4:1 Current Balun with Symmetrical Load  
(<http://www.home.earthlink.net/~christrask/Trask4to1Balun.pdf>)



# Improved 4:1 Current BALUN


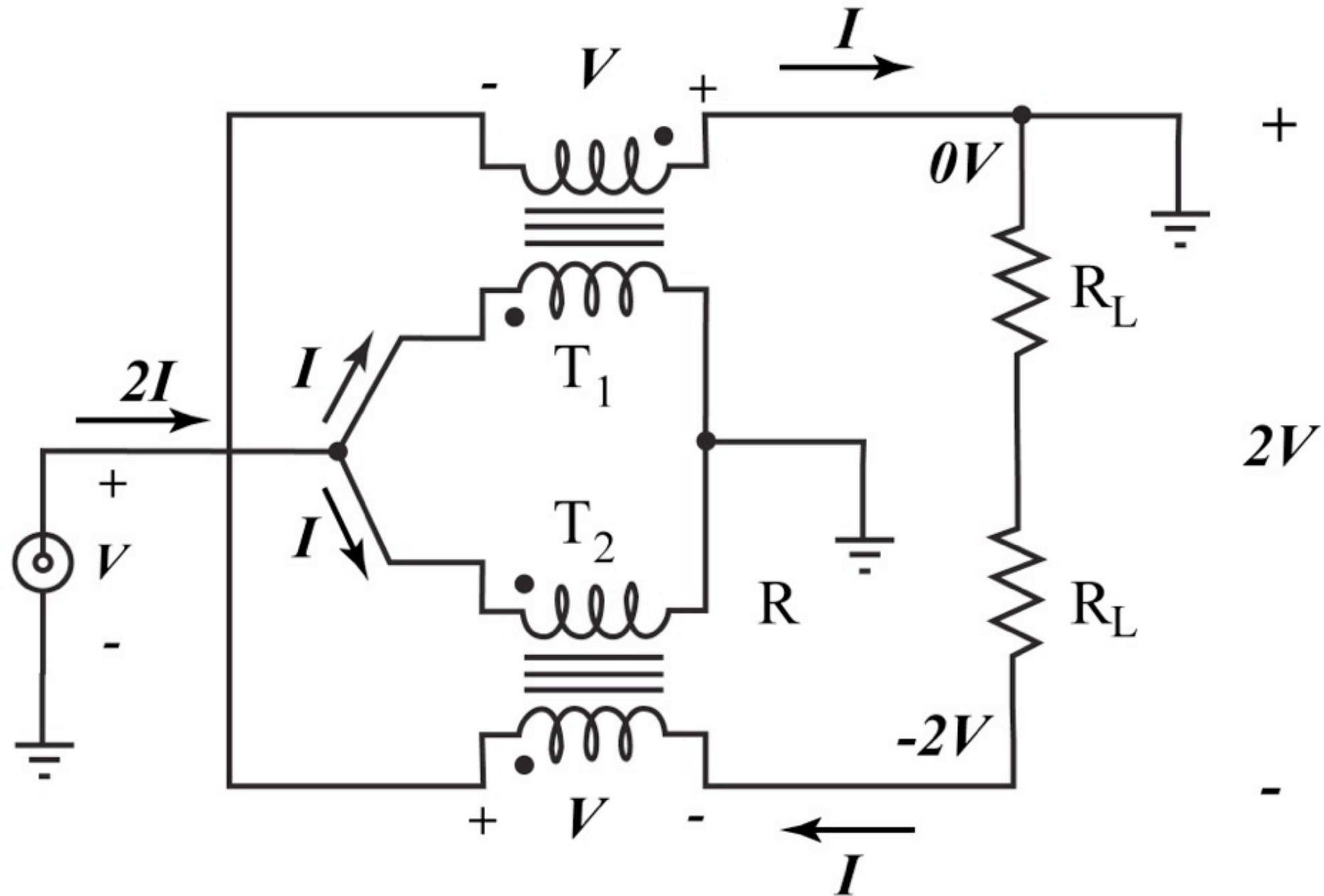


An Improved 4:1 Current Balun with Unbalanced Load  
(<http://www.home.earthlink.net/~christrask/Trask4to1Balun.pdf>)

This BALUN can be wound on a single core.



# References

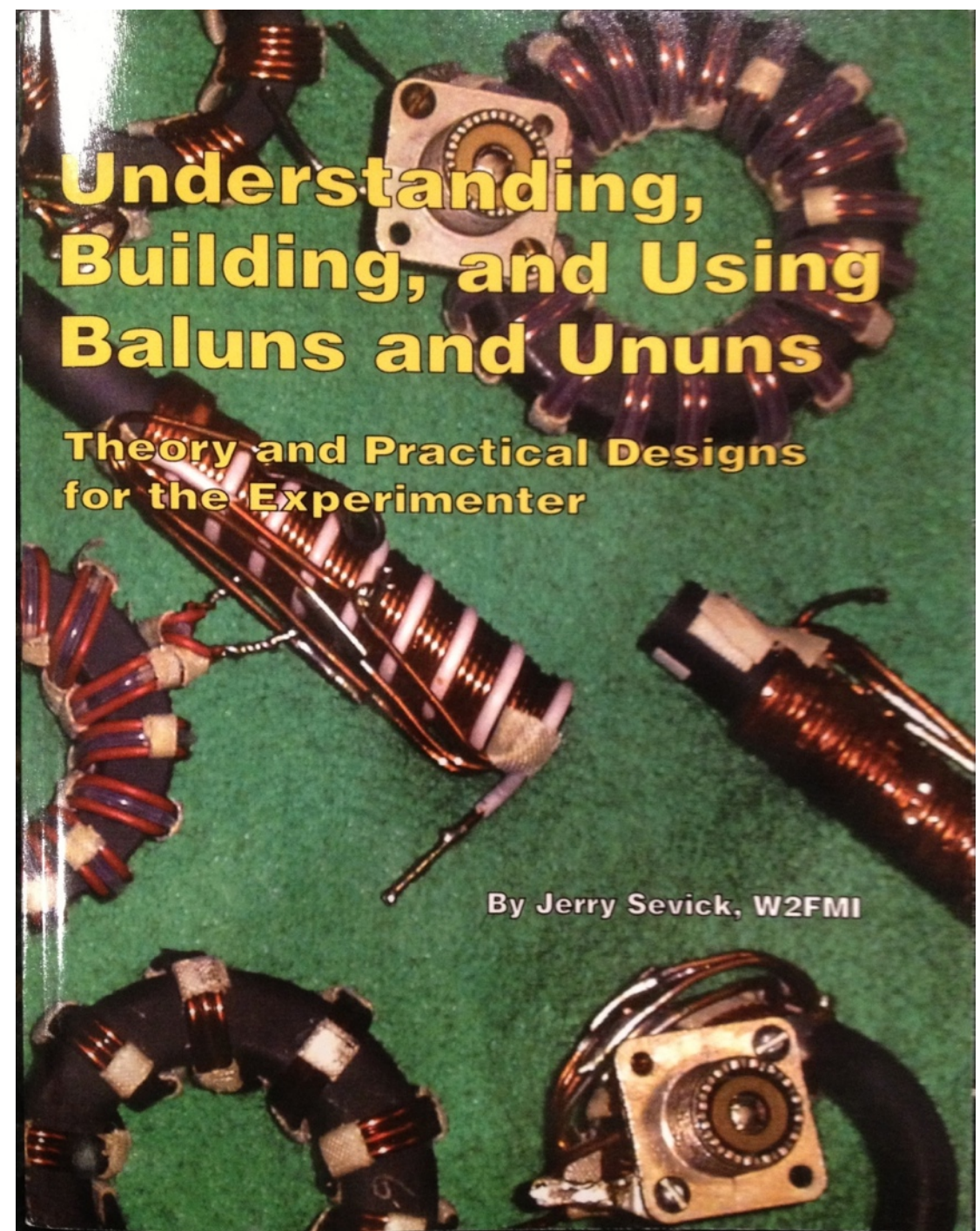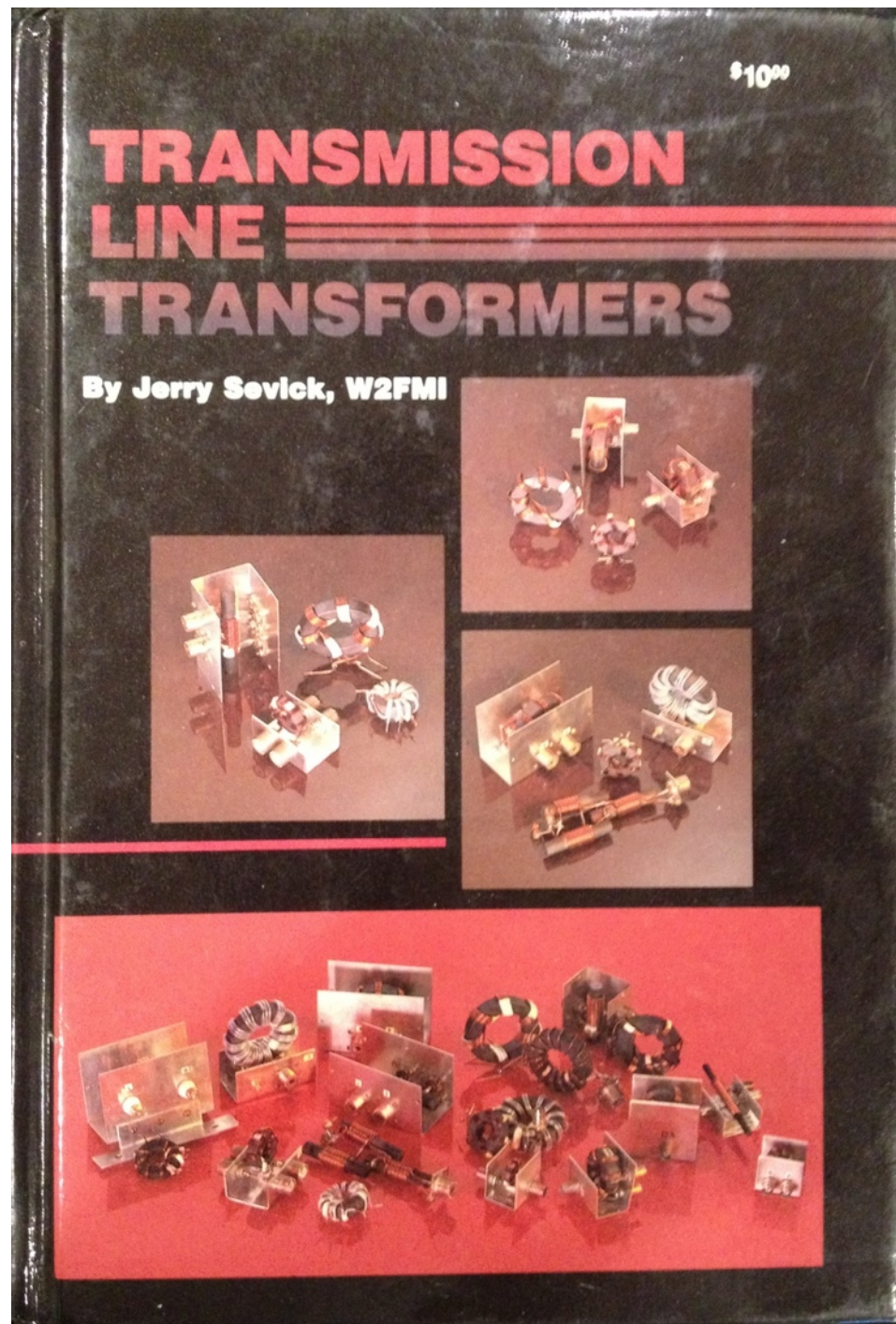

Jerry Sevick, W2FMI (SK)